

1.)Question:- Do the AC analysis of the following circuit with $C = 1600\text{pF}$, $C_1 = 80\text{pF}$, $L_1 = 312.5\text{mH}$ and $R = 1250\text{ ohm}$. Fundamental frequency for FFT is same as source frequency.

- 1) Find the resonant frequencies.
- 2) Interpret the argument plot in terms of the behaviour of circuit(region for inductive and capacitive behaviour)
- 3) Find the overall impedance of the circuit using Itspice.
- 4) Find out the components which affects resonating frequencies.
- 5) Find the harmonic components and total harmonic distortion.
- 6) Find the power factor of the circuit.

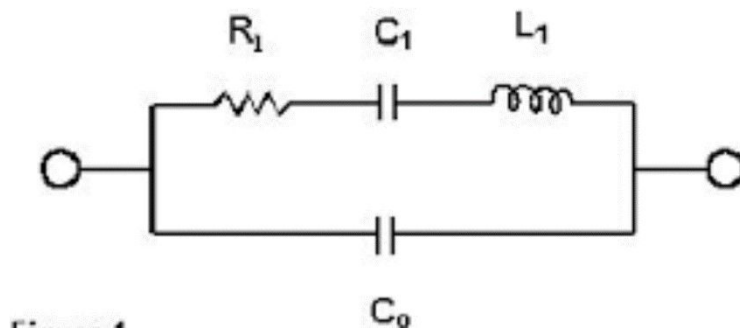


Fig Q1

2.) Design a common source amplifier which fulfills the following requirements,

- a) Load should be PMOS.
- b) Gain should be of 30 dB.
- c) Unity gain bandwidth should be of 100 MHz.